

A	B	C	D	S
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

A = Nivel de batería crítico = 1
 B = Señal GPS perdida = 1
 C = Vientos extremos = 1
 D = Obstáculos cercanos = 1

AB	00	01	11	10
00	0	0	1	0
01	0	0	0	0
11	1	1	1	1
10	0	0	0	0

$$S_1 = A \cdot B \cdot \bar{C} \cdot \bar{D}$$

$$S_2 = C \cdot D$$

$$S = (A \cdot B \cdot \bar{C} \cdot \bar{D}) + (C \cdot D)$$

$$S = (\bar{A} \cdot \bar{B} \cdot C \cdot D) + (\bar{A} \cdot B \cdot C \cdot D) + (A \cdot \bar{B} \cdot C \cdot D) + (A \cdot B \cdot \bar{C} \cdot \bar{D}) + (A \cdot B \cdot C \cdot D)$$

Logic Gates Problems 5

